

FROM RESEARCH TO INDUSTRY

cea tech

DISSIPATION IN INTEGRATED CIRCUITS AND ADIABATIC SOLUTIONS


herve.fanet@cea.fr

leti



- Limits of CMOS
- Adiabatic Solutions
- Capacitor Based Adiabatic Solutions

- Limits of CMOS
- Adiabatic Solutions
- Capacitor Based Adiabatic Solutions

More Performance... Less Power

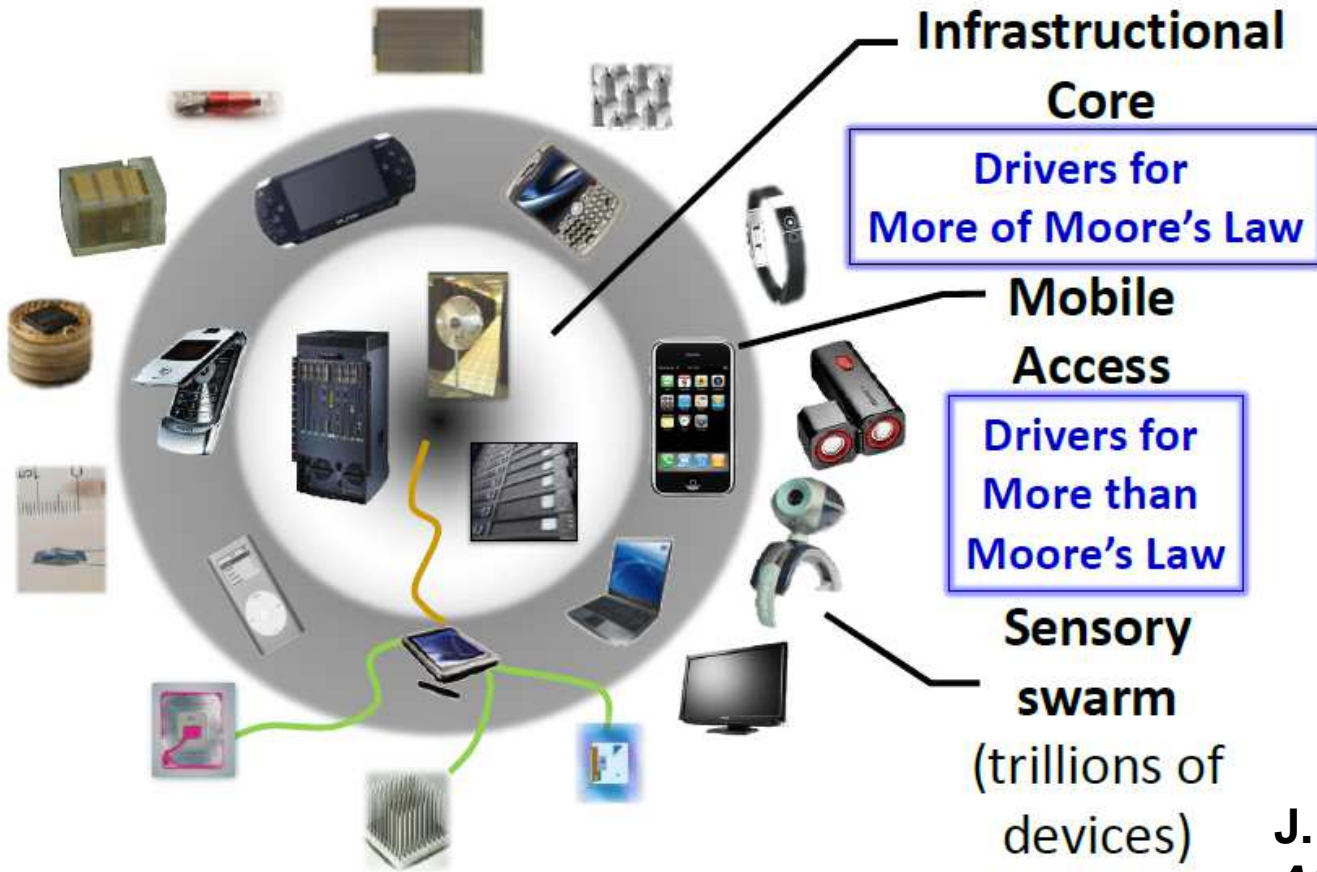


**J. Rabaey,
ASPAC 2008**

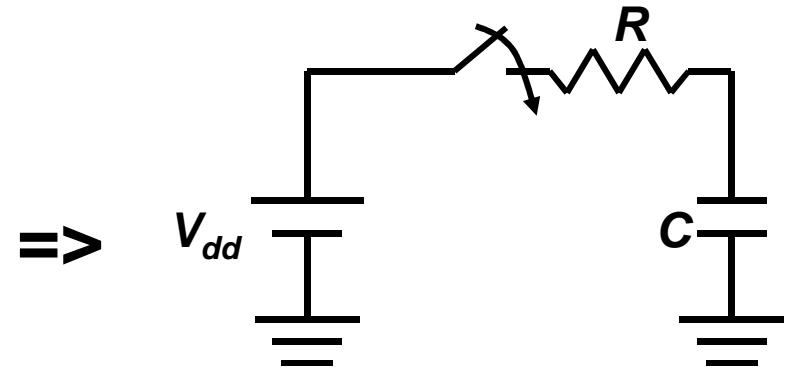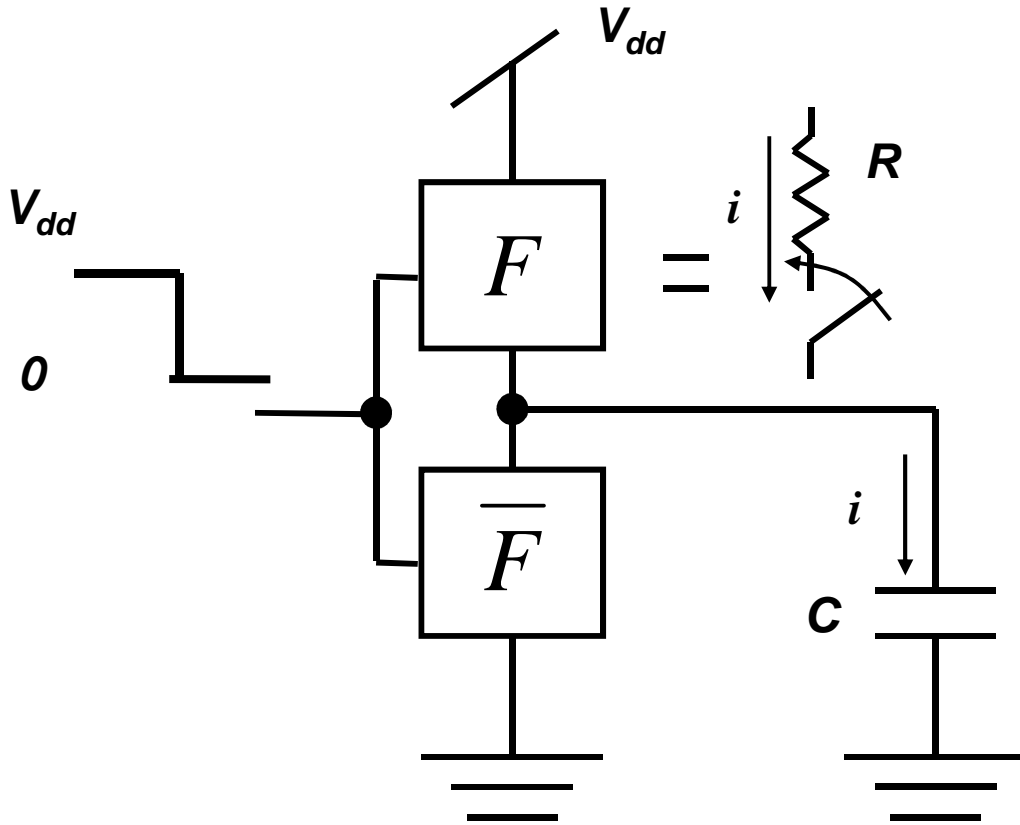

$$E_{active} = \frac{1}{2} CV_{dd}^2$$

$$E_{leakage} = V_{DD} I_{leak} T$$


CMOS VOLTAGE SCALING

 

Source: P. Packan (Intel),
2007 IEDM Short Course



POWER DENSITY VS. GATE LENGTH

 

Source: B. Meyerson (IBM)
Semico Conf., January 2004

$$E = \alpha \cdot N \cdot C \cdot k^2 \cdot n^2 \cdot v_t^2 \frac{1}{(1 - k\eta)^2} (y^2 + my \cdot e^{-y})$$

↑ $f(y)$

Normalized threshold


$$y = V_T(1 - k\eta) / nv_t$$

Overdrive factor


$$k = \frac{V_{DD}}{V_T}$$

Technology and architecture dependent parameter
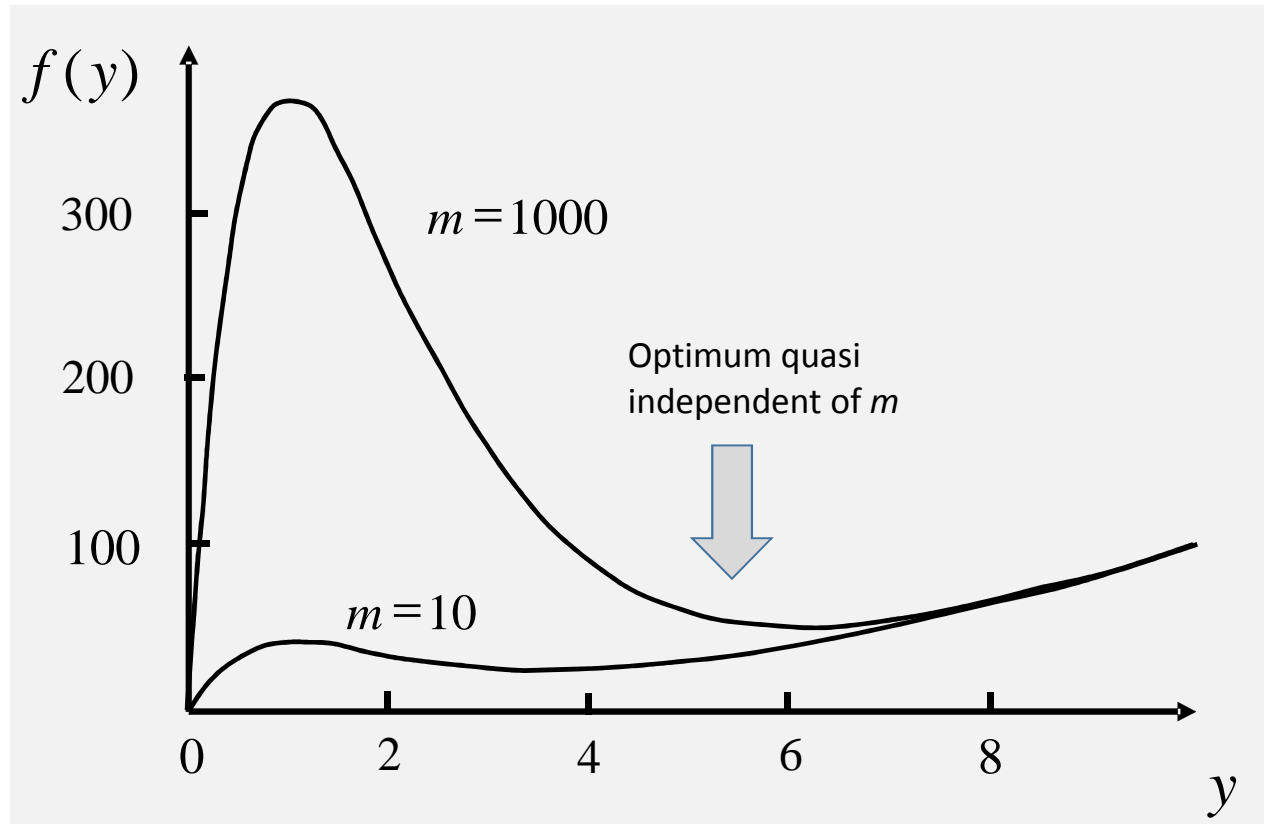
$$m = \frac{Tv_t}{\alpha nk} \cdot \frac{WC_{ox}}{LC} \mu \cdot e^{1.8} \cdot (1 - k\eta)$$



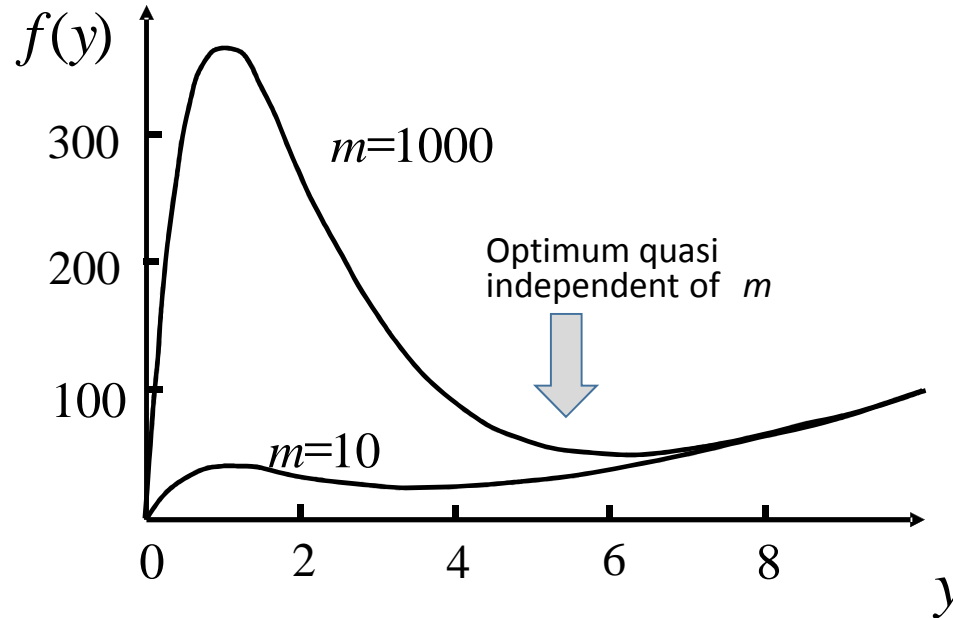V_T optimal around 200 mV independently of technology and architecture



V_T optimal around 200 mV independently of technology and architecture



V_{DD} optimal around 600 mV for high performance regime

V_{DD} optimal around 400 mV for near-threshold regime

V_{DD} optimal around 250 mV for sub-threshold regime


No solution for ultra low power with CMOS

  - Limits of CMOS
- **Adiabatic Solutions**
- Capacitor Based Adiabatic Solutions



$$E_{adiabatic} \cong \frac{RC}{T} CV_{dd}^2$$


V_{DD} constant

 

Conventional Logic

$$E = CV_{DD}^2 + leakage$$

V_{DD} not constant

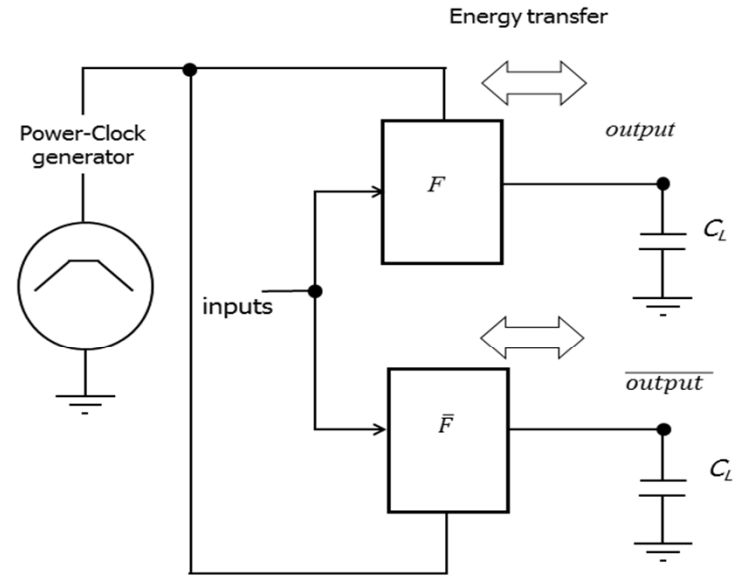

Adiabatic Logic

$$E = \frac{2RC}{T} CV_{DD}^2 + leakage$$




BUT INPUTS HAVE TO BE STABLE DURING RAMP-UP AND RAMP-DOWN

Optimal (for dissipation) charge and discharge of capacitances : the adiabatic mode

Retractable logic solution

Quasi-adiabatic pipeline

Reversible pipeline

   


CMOS: $\frac{RC}{T} CV_{DD}^2 + leakage$


CMOS: $CV_T^2 + \frac{RC}{T} CV_{DD}^2 + leakage$

CMOS: $\frac{RC}{T} CV_{DD}^2 + leakage$

P. Teichmann, 2012

 


a)

 

b)

 Inverter circuit in the (a) PFAL and (b) ECRL family






Adiabatic

Non-Adiabatic

Leakage
 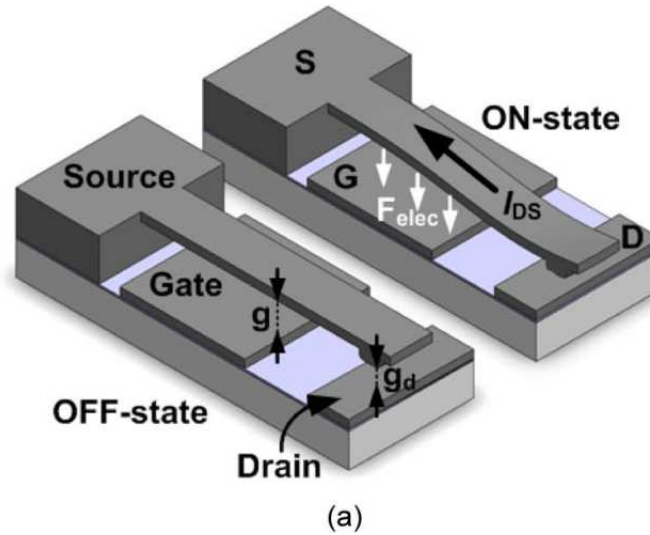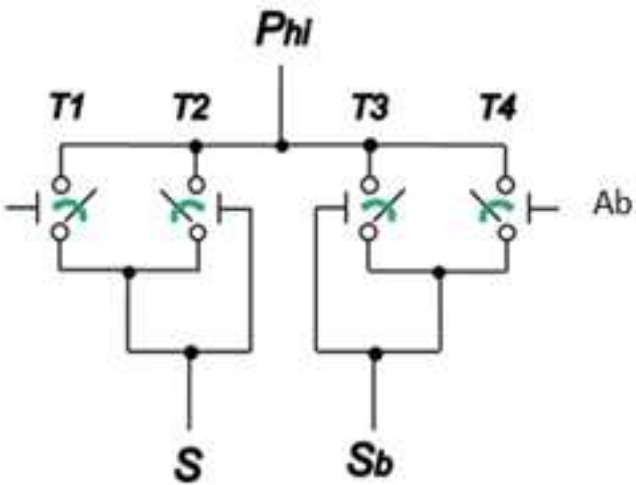
$$E_{dissipated} \cong 2 \frac{RC}{T} CV_{dd}^2 + \frac{1}{2} CV_T^2 + I_{leakage} V_{dd} T$$



$$E = 2 \frac{R \cdot C_L}{T} C_L \cdot V_{dd}^2 + \frac{1}{2} C_L \cdot V_{RL}^2$$


CMOS

$$E_{dissipated} \cong 2 \frac{R_{cmos} C_L}{T} C_L V_{dd}^2 + \frac{1}{2} C_L V_T^2 + I_{leakage} V_{dd} T$$

NEMS
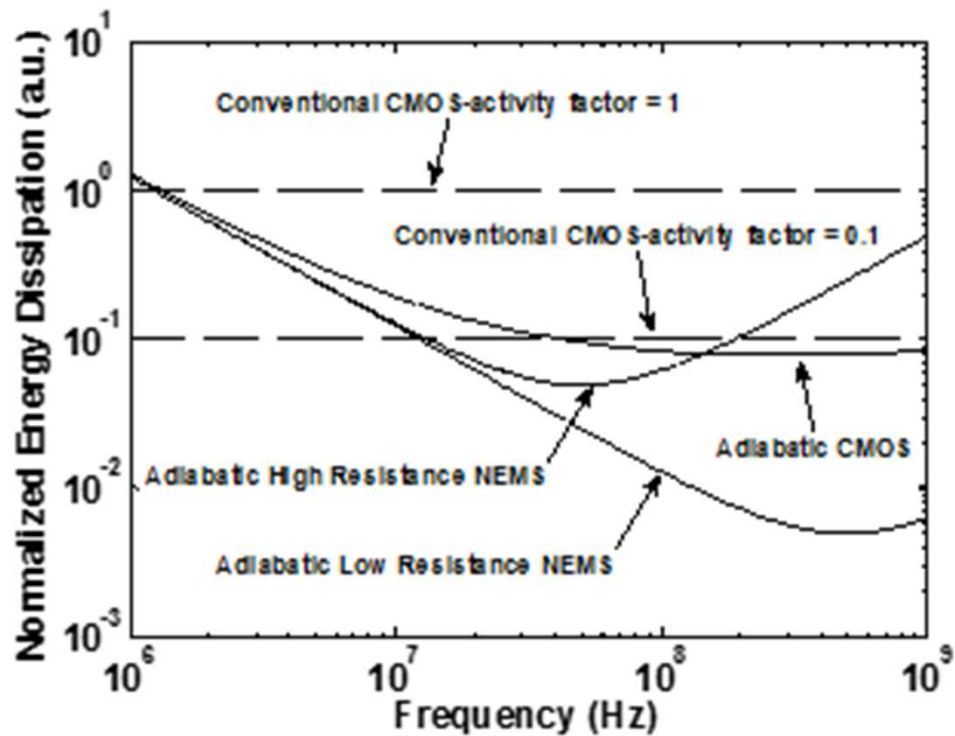
$$E_{dissipated} = 2 \frac{R_{nems} \cdot C_L}{T} C_L \cdot V_{dd}^2 + \frac{1}{2} C_L \cdot V_{RL}^2 + 0$$






Strong effect of contact resistance

Contact technology is challenging

- Limits of CMOS
- Adiabatic solutions
- **Capacitor Based Adiabatic solutions**

Constant supply voltage

 


Conventional CMOS

$$E = \frac{1}{2} CV_{DD}^2$$

Leakage


Variable supply voltage

 


Adiabatic CMOS

$$E = \frac{R_P C}{T} CV_{DD}^2 + CV_T^2$$

Leakage

 


Variable supply voltage

 


Adiabatic
Capacitor based Logic

$$E = \frac{r_i C}{T} CV_{DD}^2$$

Zero leakage

 
 
$$V_s(t) = \frac{R_n(t)}{R_n(t) + R_p(t)} V_{DD}(t)$$




$$C \frac{d(V_{DD} - V_s)}{dt} + (V_{DD} - V_s) \frac{dC}{dt} = C_L \frac{dV_s}{dt}$$

$$\frac{d}{dt}(CV_{DD}) = -\frac{d}{dt}(C_L V_s) + \frac{d}{dt}(CV_s)$$

$$V_s(t) = \frac{C(t)}{C(t) + C_L} V_{DD}(t)$$

- Electrode geometry variation
- Permittivity variation

Microcapacitor example

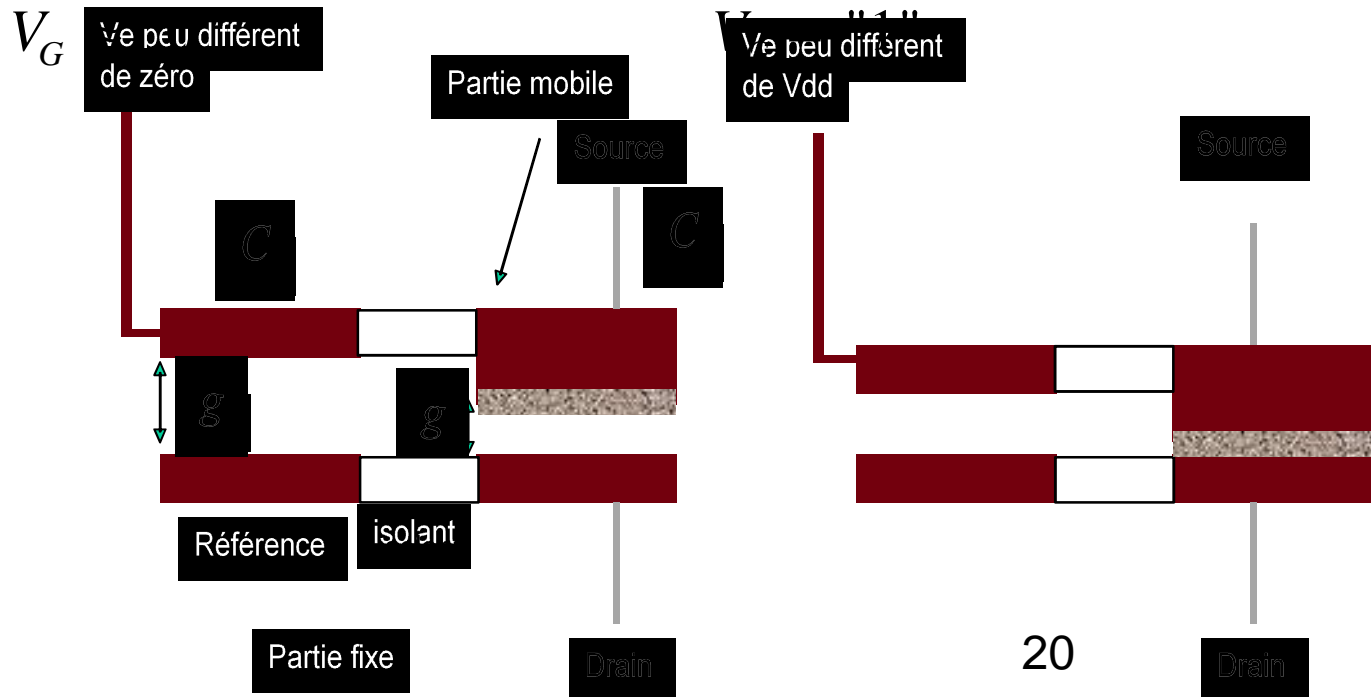

- Adiabatic principle is « the » solution for ultra low power
- Reversible logic not necessary in a first step
- Choice of technology not yet clear but capacitor based logic seems promising